
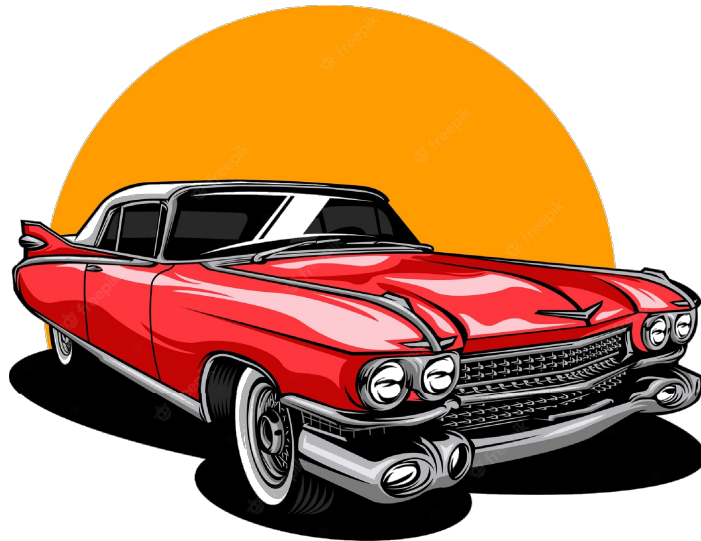


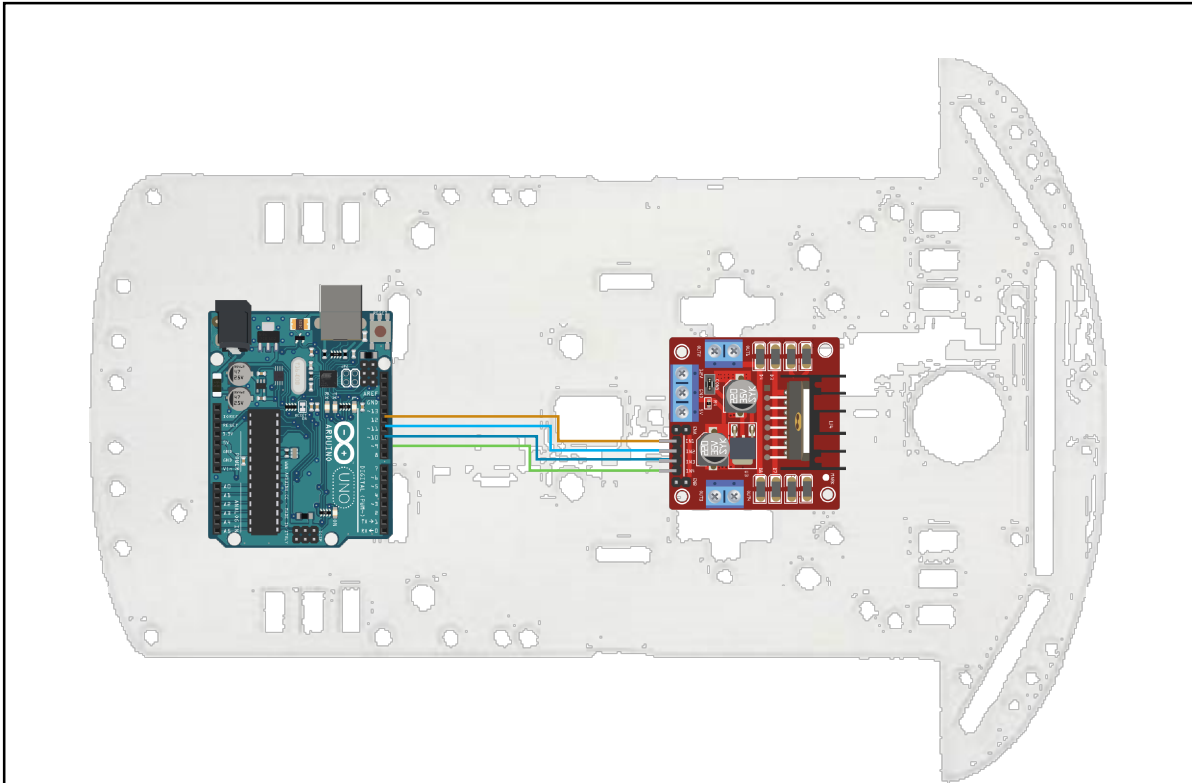Smart Mobile Remote Controlled Car Kit 1.0 Plus



Connection Diagram


Step 1 : Arduino UNO, L298N Motor Driver



Connection Table

Arduino UNO	L298N Motor Driver
12 Pin	IN 1
11 Pin	IN 2
10 Pin	IN 3
9 Pin	IN 4

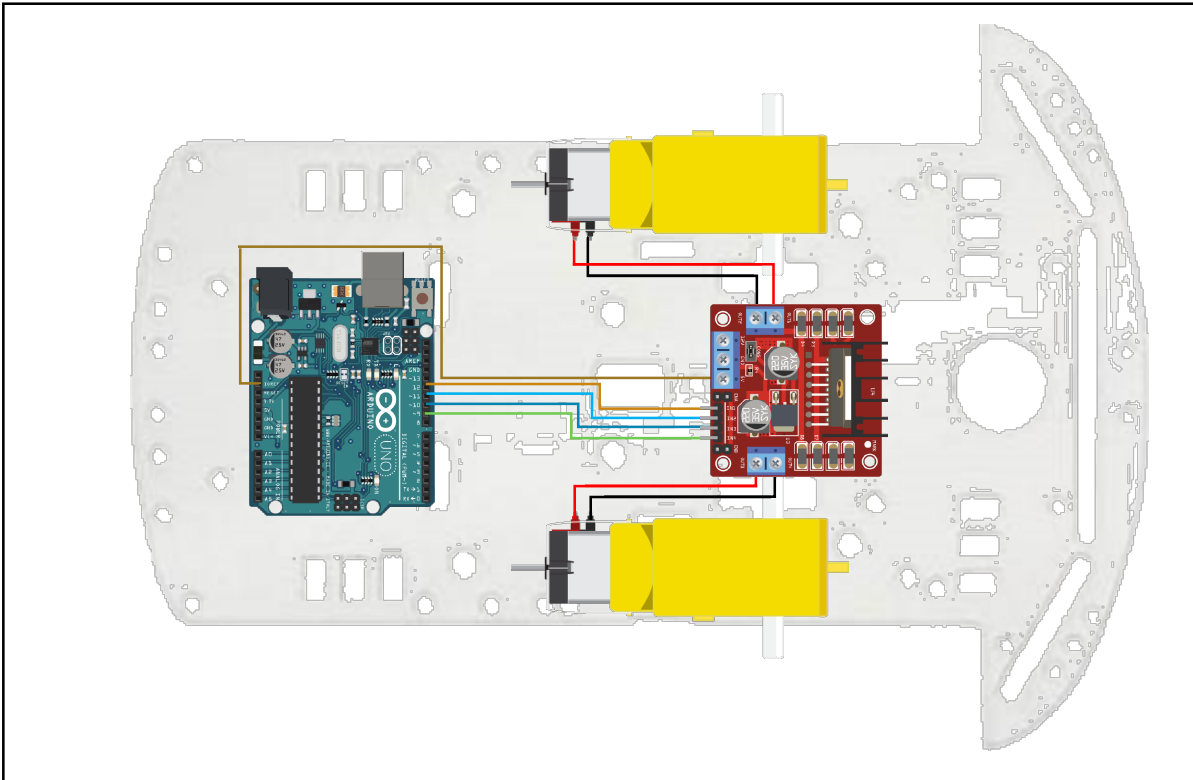
Step 2 : Motor A, Motor A and L298N Motor Driver



Connection Table

Motor A	L298N Motor Driver
Terminal 1	Out 1
Terminal 2	Out 2
Motor B	L298N Motor Driver
Terminal 1	Out 3
Terminal 2	Out 4

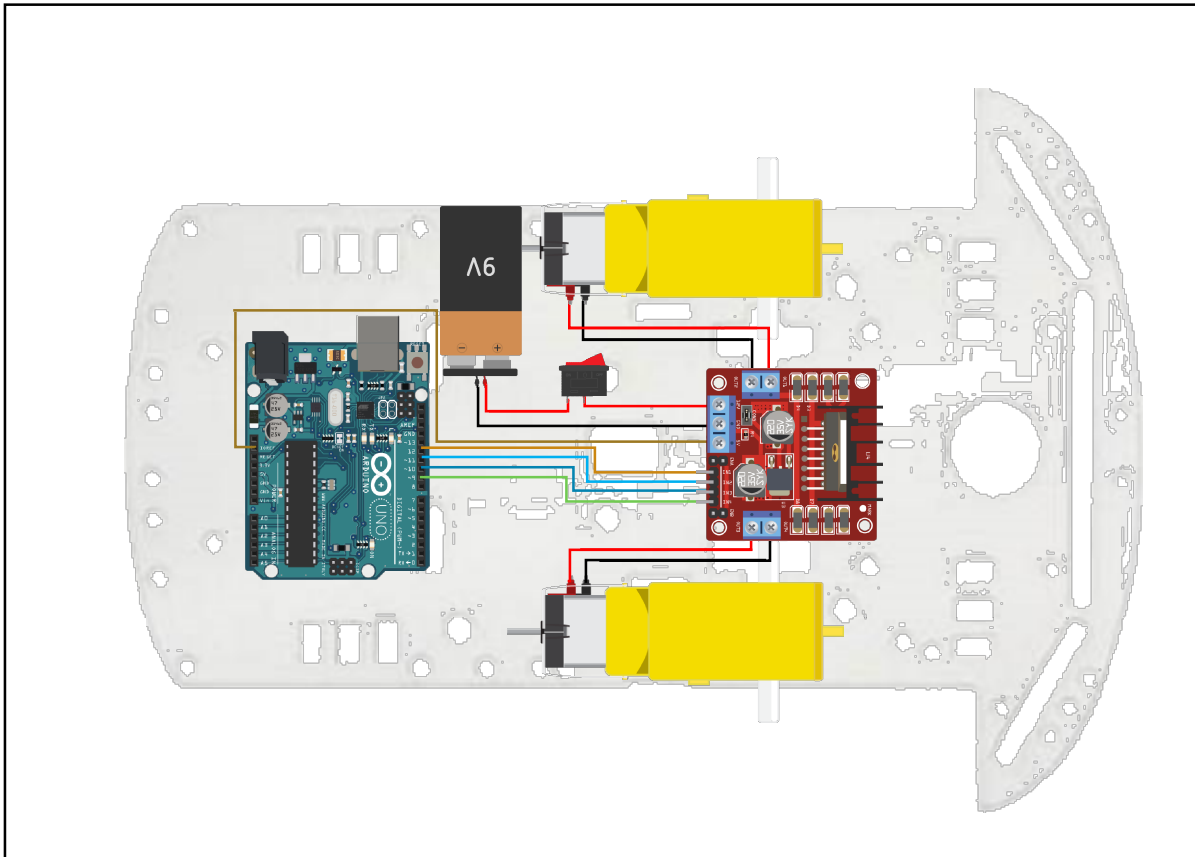
Step 3 : 9 V Battery A, Arduino UNO, L298N Motor Driver



Connection Table

9 V Battery A	L298N Motor Driver
(-)	GND
(+)	+12 Volt
Arduino UNO	L298N Motor Driver
(+5 Volt)	+5 Volt


Step 4 : Arduino UNO and HC-05 Bluetooth

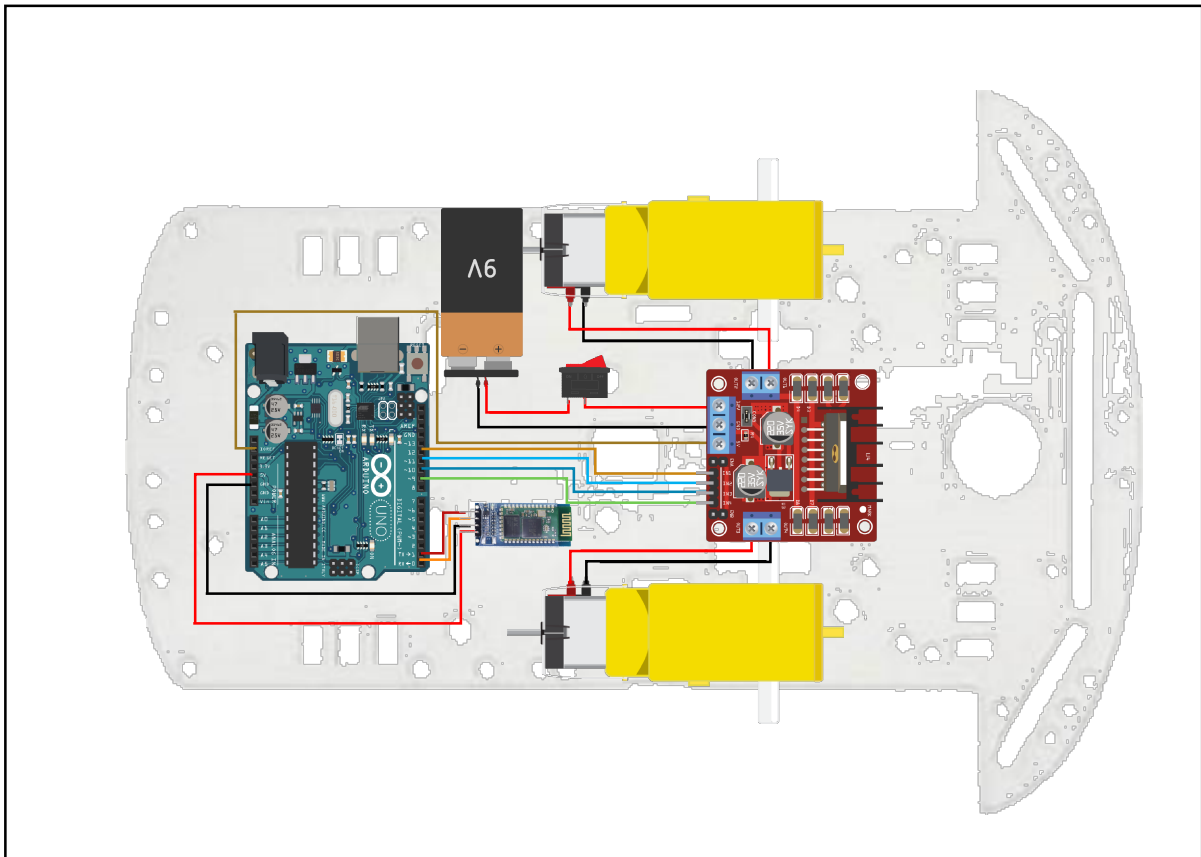

Connection Table


Arduino UNO	HC-05 Bluetooth
(+5V)	VCC
GND	GND
TX Pin	RX Pin
RX Pin	TX Pin

Step 5 : Arduino Uno ,9 V Battery B

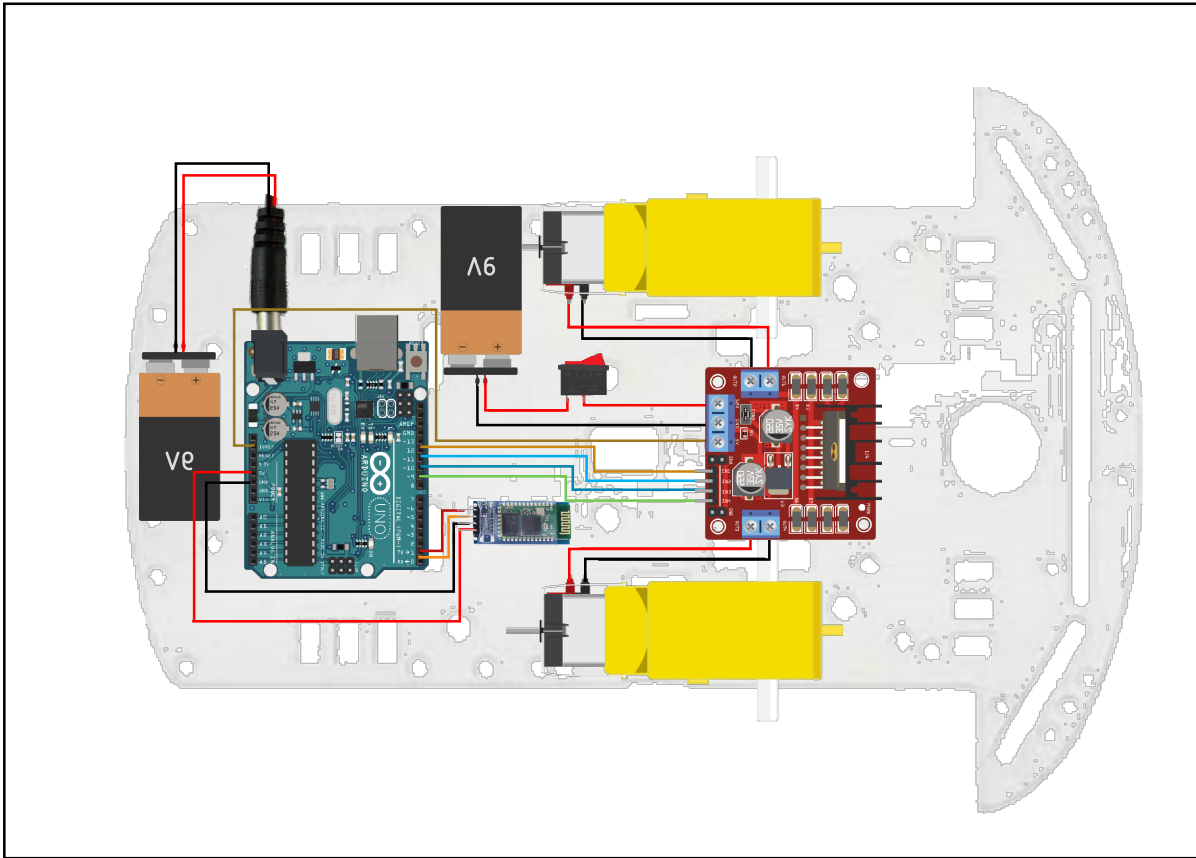

Connection Table	
Arduino UNO	9 V Battery B
DC power port	Snap Connector

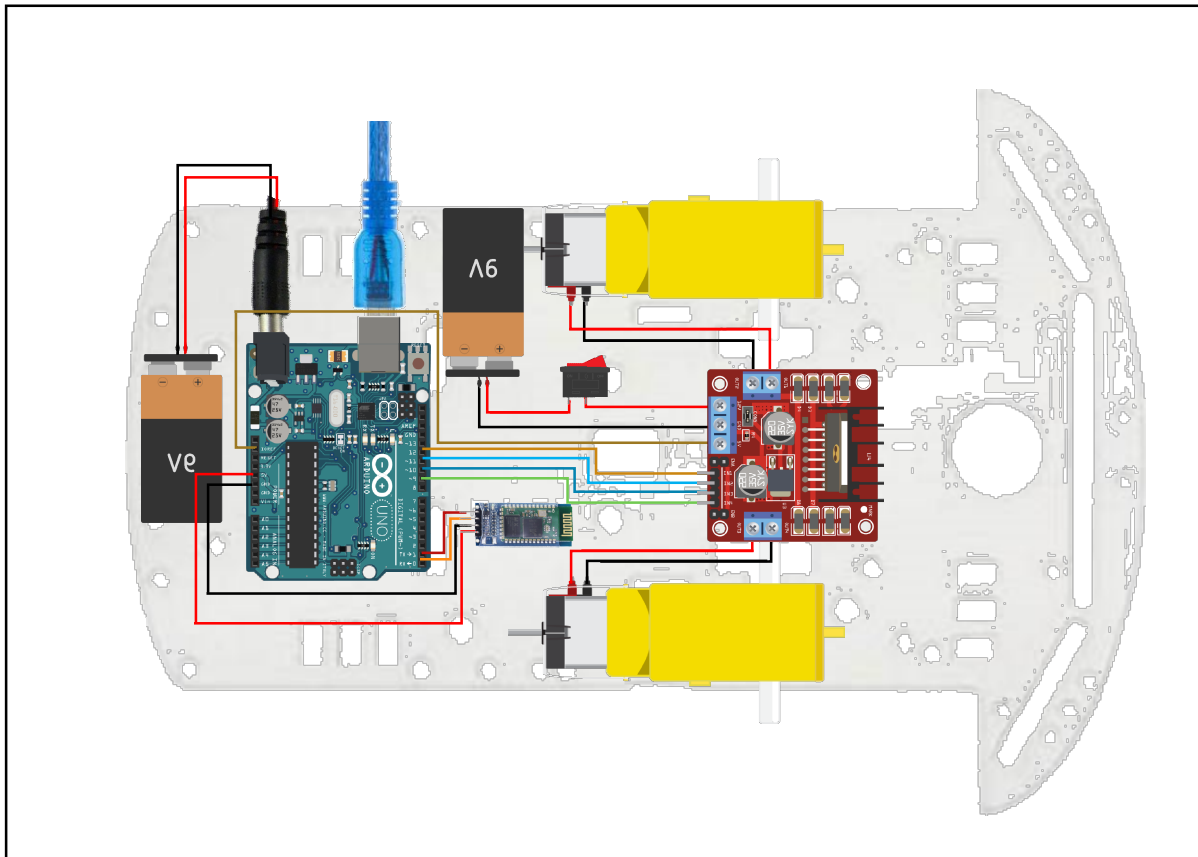Step 6 : Arduino Uno ,USB cable connection with laptop /PC



Connection Table	
Arduino UNO	USB cable connection with laptop /PC
USB type B port	USB cable